

Digital to Analog Converter

Jungchul Lee
Kamran Jeelani
Jonathan Beckwith

Topics of Discussion

- What is a DAC?
- Types of DAC Circuits
 - Resistor-string DAC
 - N-Bit Binary weighted DAC
 - R-2R Ladder DAC
- Specifications of DAC
- Applications

What is a DAC?


- Digital-to-Analog Converter: An electronic device, often an integrated circuit, that converts a digital number into a corresponding analog voltage or current.
- Relation between analog signal and digital equivalent

$$V_a = \sum_{i=1}^n b_i 2^{-i} \times V_{\text{ref}}$$

- AD conversion – $V_a \rightarrow b_i$ (encoder) ex) Transducer interface
- DA conversion – $b_i \rightarrow V_a$ (decoder) ex) motor, heater control

DAC configurations


- Assume the analog signal is a voltage

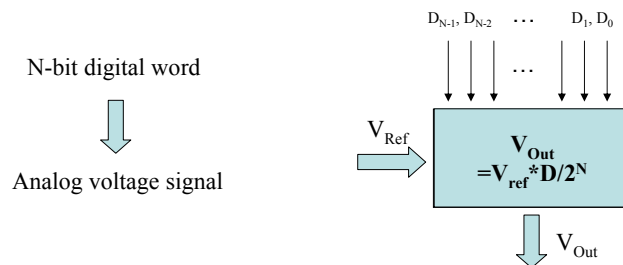

Types of DAC Circuits

1. Resistor-string
2. N-Bit Binary Weighted Resistor
3. R-2R Ladder

A Resistor-string DAC

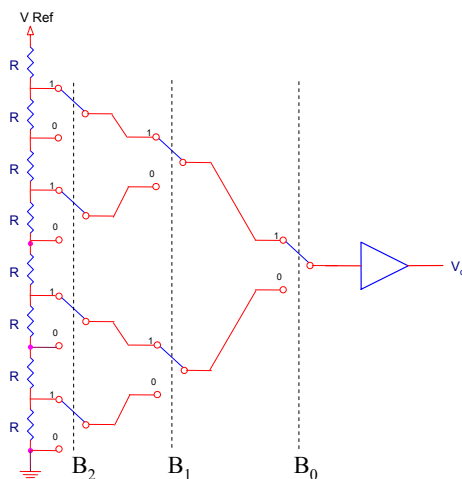

Example of 3 bit resistor-string DAC

Required component

- a resistor string
- a set of switches – select output to use
- opamp – buffer

$$V_0 = V_{Ref} \sum_{i=0}^{N-1} \frac{b_i}{2^{i+1}}$$

Resistor String DAC Example


- How many resistors and switches would be required to implement an 8 bit resistor-string DAC?

Ans) # of resistors = $2^N = 2^8 = 256$

of switches = $\sum_{i=0}^{N-1} 2^i = 2^8 - 1 = 255$

Impractical for converters with more than a few bits of resolution

N-Bit Binary Weighted Resistor

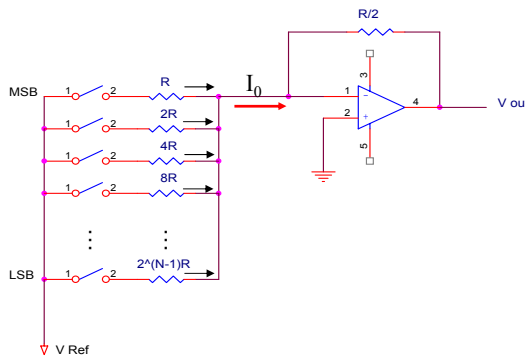

$$I_0 = V_R \sum_{i=1}^N \frac{b_i}{2^{(i-1)} R}$$



$$V_0 = -R_f I_0$$


N-bit binary weighted Example

- Find output voltage, current, and resolution for a binary weighted resistor DAC of 4 bits
 - given condition

$$R = 10 \text{ k}\Omega, R_f = 5 \text{ k}\Omega, V_R = -10 \text{ V}$$

Applied binary word is 1001

Example Solutions

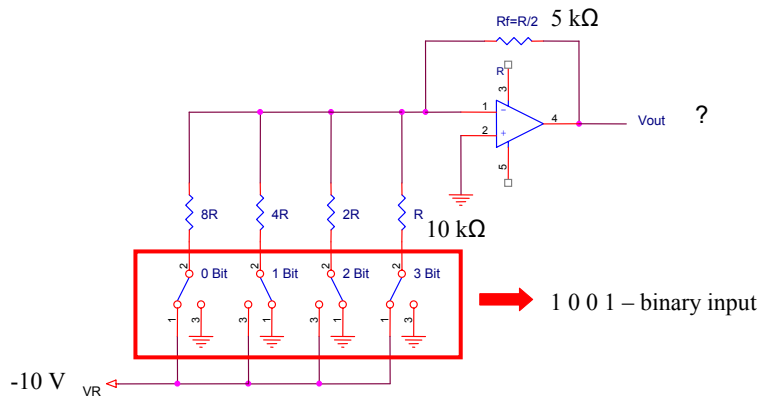

Example Solutions (Cont.)

Ans)


$$I_0 = \frac{-10 \text{ V}}{\Omega} \left[\frac{1}{2^0 \times 10^4} + \frac{0}{2^1 \times 10^4} + \frac{0}{2^2 \times 10^4} + \frac{1}{2^3 \times 10^4} \right]$$

$$= -0.001125 \text{ A}$$

$$V_0 = -R_f I_0 = -(5 \times 10^3 \Omega) \times (-0.001125 \text{ A}) = 5.625 \text{ V}$$

$$\text{Resolution} = \text{LSB} = \frac{V_{\text{Ref}}}{2^n} = \frac{10 \text{ V}}{2^4} = 0.625 \text{ V}$$

Example Solutions (Cont.)

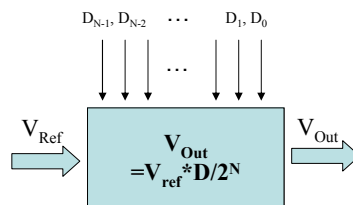

- Binary Word input = $1001_2 = 9_{10}$
- # of input combination : $2^4 = 16$
- $V_{\text{out}} = V_{\text{ref}} * D / 2^N = 10 * 9 / 16 = 5.625 \text{ V}$

Limitations of the Binary Weighted DAC

1. If $R = 10 \text{ k}\Omega$, 8 bits DAC, and $V_{\text{Ref}} = 10 \text{ V}$

$$R_8 = 2^{8-1} * (10 \text{ k}\Omega) = 1280 \text{ k}\Omega$$

$$I_8 = V_{\text{Ref}}/R_8 = 10\text{V}/1280 \text{ k}\Omega = 7.8 \mu\text{A}$$

Op-amps that can handle those currents are rare and expensive.


2. If $R = 10 \Omega$ and $V_{\text{Ref}} = 10 \text{ V}$

$$R_1 = 2^{1-1} * (10 \Omega) = 10 \Omega$$

$$I_1 = V_{\text{Ref}}/R_1 = 10\text{V}/10 \Omega = 1 \text{ A}$$


This current is more than a typical op-amp can handle.

R-2R Resistor Ladder DAC

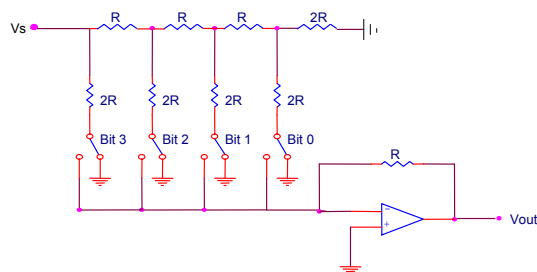


- Simplest type of DAC
- Requires only two precision resistance value (R and $2R$)

R-2R Resistor Ladder DAC

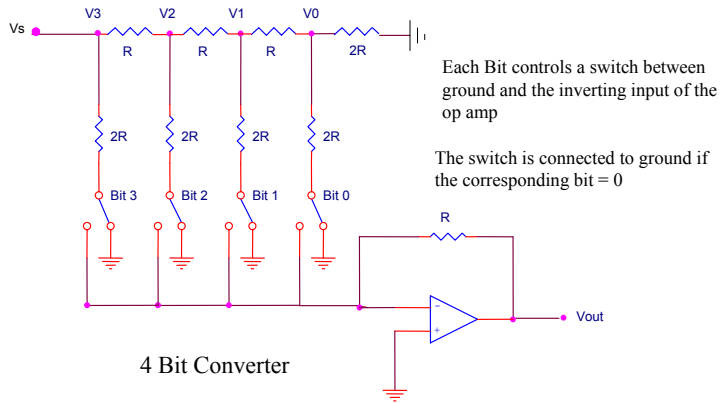


R-2R DAC Example


Ex. Convert 0001 to analog

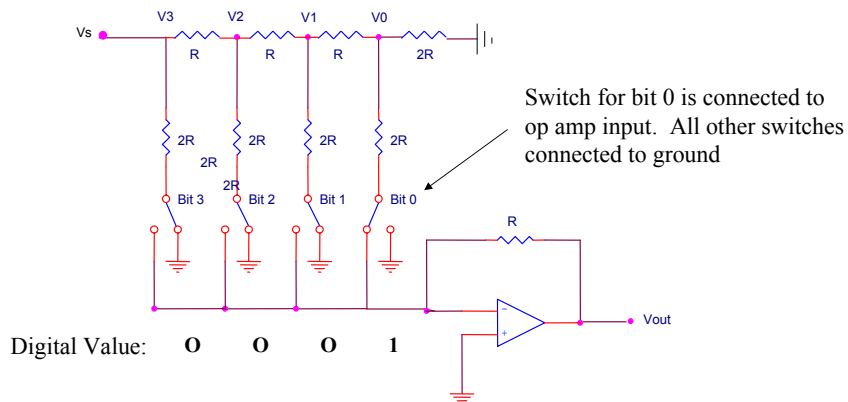

R-2R DAC Example (cont.)

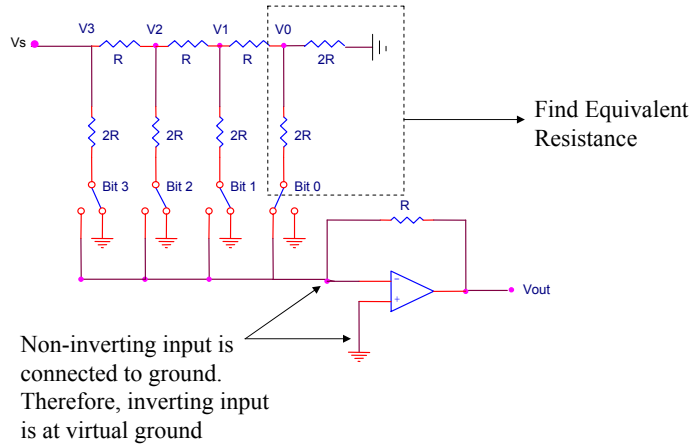


R-2R DAC Example (cont.)

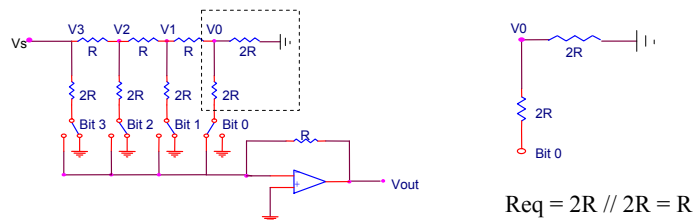

Apply voltage division:

$$V_0 = V_1 \times \frac{Req}{(Req+R)} \longrightarrow V_0 = \frac{1}{2} V_1$$

R-2R DAC Example (cont.)

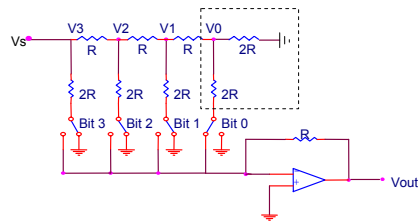

We have shown that $V_0 = \frac{1}{2} V_1$


Similarly, It can be proven that :

$$V_1 = \frac{1}{2} V_2 \quad \text{AND} \quad V_2 = \frac{1}{2} V_3$$

Therefore:

$$V_0 = \frac{1}{8} V_3 = \frac{1}{8} V_s$$

R-2R DAC Example (cont.)

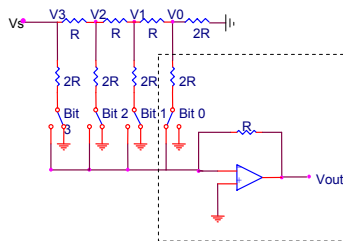

V_0 is the input to the inverting amplifier circuit, which has a gain of:

$$A_v = -R/2R = -1/2$$

Therefore, the analog output voltage corresponding to the binary input 0001 is:

$$\begin{aligned} V_{out_0} &= A_v (V_0) \\ &= (-1/2)(1/8 * V_s) \end{aligned}$$

$$V_{out_0} = -1/16 V_s$$

R-2R DAC Example (cont.)

We have shown that the analog output voltage for the digital input 0001 is:

$$V_{\text{out}0} = -1/16 \text{ Vs}$$

Similarly, it can be show that:

For input = 0010: $V_{\text{out}1} = -1/8 \text{ Vs}$

For input = 0100: $V_{\text{out}2} = -1/4 \text{ Vs}$

For input = 1000: $V_{\text{out}3} = -1/2 \text{ Vs}$

The output for any combination of bits comprising the input binary number can now be found using the principle of superposition:

$$V_{\text{out}} = b_3 V_{\text{out}3} + b_2 V_{\text{out}2} + b_1 V_{\text{out}1} + b_0 V_{\text{out}0}$$

General DAC Characteristics

There are six key parameters you should consider when choosing a DAC.

- Reference Voltage
- Resolution
- Linearity
- Speed
- Settling Time
- Error

Reference Voltage

To a large extent, the characteristics of a DAC are defined by its reference voltage.

- Non-multiplier DAC: V_{ref} is fixed (specified by the manufacturer)
- Multiplier DAC: V_{ref} is provided via an external source

Full Scale Voltage

Defined as the output when the digital input word is all 1's.

$$V_{fs} = V_{ref} \left(\frac{2^N - 1}{2^N} \right)$$

Resolution

Resolution is a measure of precision, not accuracy. It is defined as the voltage change corresponding to changing the LSB.


- Many options in the 8-16 bit range, with 12 bits being a typical cost / resolution trade off.
- More bits \longrightarrow More steps \longrightarrow Greater Resolution

$$\text{Resolution} = V_{\text{LSB}} = V_{\text{Ref}} / 2^N$$

*where N is the number of bits

Linearity

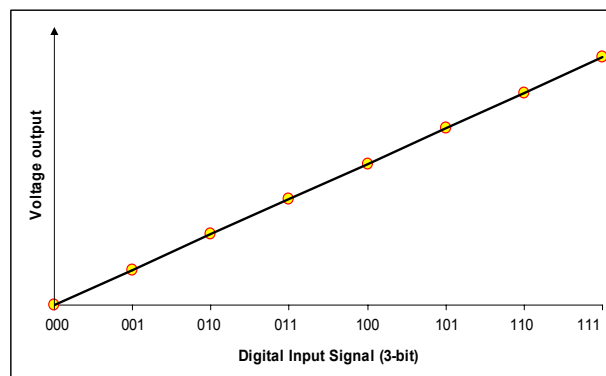- Ideally, a DAC will produce a linear relationship between a binary word and analog output



Speed


Usually specified as conversion or sampling rate.

- High speed DACs are typically defined as $>1\text{MS/s}$ (1Mhz)
- Some current 12-16 bit DACs can reach the 1GHz range
- Conversion of input signal is limited by
 - Clock speed of the input signal
 - Settling time of the DAC

Settling Time


- Ideally, an instantaneous change in analog voltage would occur when a new binary word enters into a DAC.
- Settling time is the time taken by the DAC to reach $\frac{1}{2}$ of the LSB of its new voltage.
- Components include delay, slew time, and ring time.
- Fast converters reduce slew time, but usually result in longer ring times.
- Delay time is normally a small term.

Settling Time (cont.)

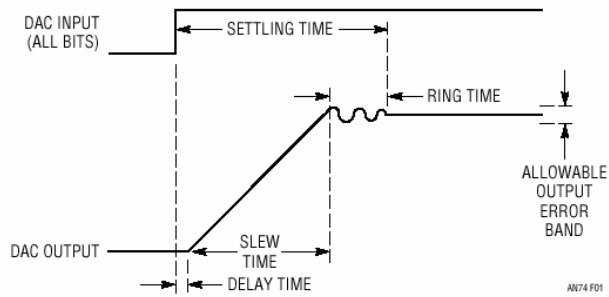

Cause of Delay Time, Settling Time, and Ring Time

R-2R Resistor Ladder DAC

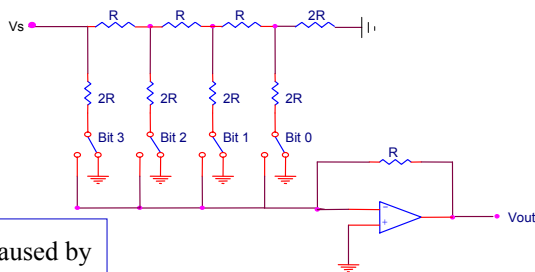

Delay time is caused by the time it takes to change these switches based on input bits.

Settling time and Ring time is determined by the op-amp's slew rate


Possible Error

Because we do not live in an “ideal” world, considerations for possible error should be made.

- Non-Linearity
 - Integral
 - Differential
- Non Monotonicity
- Offset Error
- Gain Error


Integral Non-linearity

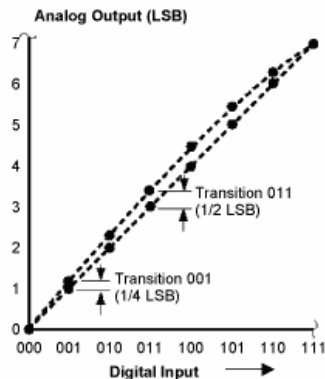- Defined as the deviation of a DAC's transfer function from a straight line.
- The straight line can be a best approximation to the actual transfer function, or a line drawn between the transfer function's end points (after subtracting the gain and offset errors)




Differential Non-Linearity

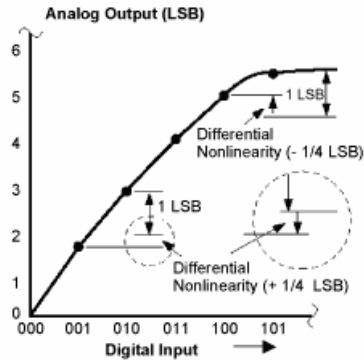- The difference between an actual step height and the ideal value of 1LSB.
- Should be less than or equal to one to insure monotonicity.




Non-Monotonicity

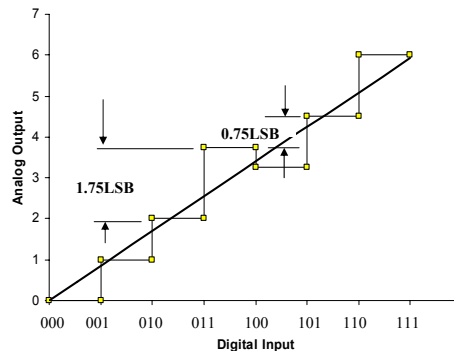- A monotonic DAC yields an increase in output as input increases.
- If a differential non-linearity of greater than 1LSB occurs, increasing the digital input may actually result in a decreased output.




Gain Error

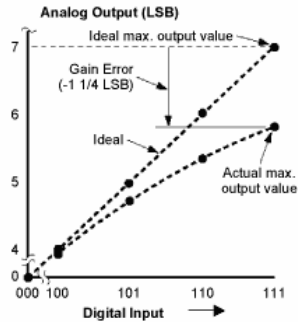- Defined as the difference between the ideal max output voltage and the actual max output voltage (after subtracting offset error).
- Changes the slope of the output, thereby creating the same percentage error for each step.
- Expressed in mV as a percentage of the maximum output.




Offset Error

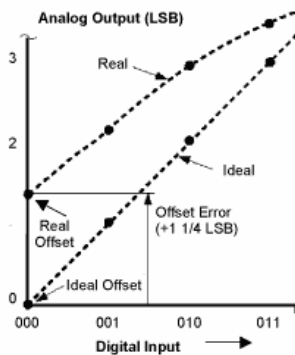- The offset error equals the analog output when the digital signal is zero.
- Typically defined in absolute millivolts with (10mV being acceptable).



Cause of Non-Linearity, Gain error, and Offset error

R-2R Resistor Ladder DAC

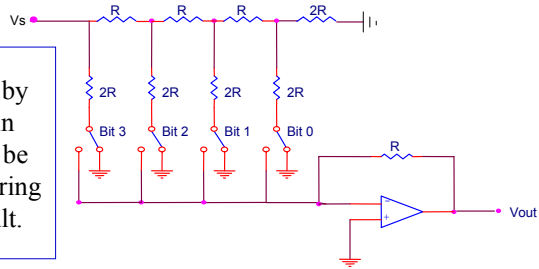

Non-linearity is caused by the resistors. Resistors in D/A converters need to be matched but manufacturing exact resistors is difficult.

Gain Error and Offset Error is caused by op-amp and or op-amp's feedback resistor

DAC Applications

- DAC's can be found in any device that interfaces digital and analog circuitry
- Analog Displays
- Digital Control Systems
- Digital Audio
- Communications
- Countless other applications

References

- **Digital-Analog Converters Are a "Bit" Analog – Maxim Semiconductors**
(http://www.maxim-ic.com/appnotes.cfm/appnote_number/1055/ln/en)
- **Component and Measurement Advances Ensure 16-Bit DAC Settling Time**
– Jim Williams, Linear Technology July 1998
- **Introduction to Mechatronics and Measurement systems – David G. Alciatore and Michael B. Hstand, McGrawHill**
- **Mechatronics-Electronic control systems in mechanical and electrical engineering-W. Bolton, Longman**
- **Introduction to Electronic Circuit Design-Richard R. Spencer and Mohammed S. Ghausi, PrenticeHall**

Questions ??